

Writeup Minju Kang

First, I started with testing the given test bench with behavioral decoder.

<Behavioral>


```
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog decoder.v
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog decoder.t.v
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
En A0 A1| 00 01 02 03 | Expected Output
0 0 0 | 0 0 0 0 | All false
0 1 0 | 0 0 0 0 | All false
0 0 1 | 0 0 0 0 | All false
0 1 1 | 0 0 0 0 | All false
1 0 0 | 1 0 0 0 | 00 Only
1 1 0 | 0 1 0 0 | 01 Only
1 0 1 | 0 0 1 0 | 02 Only
1 1 1 | 0 0 0 1 | 03 Only
```

Then, I built the structural decoder with 2 NOT gates and 8 AND gates (4 for inputs and 4 for inputs & enable).

<Structural>

```
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog decoder.t.v
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
VCD info: dumpfile decoder.vcd opened for output.
En A0 A1| 00 01 02 03 | Expected Output
0 0 0 | 0 0 0 0 | All false
0 1 0 | 0 0 0 0 | All false
0 0 1 | 0 0 0 0 | All false
0 1 1 | 0 0 0 0 | All false
1 0 0 | 1 0 0 0 | 00 Only
1 1 0 | 0 1 0 0 | 01 Only
1 0 1 | 0 0 1 0 | 02 Only
1 1 1 | 0 0 0 1 | 03 Only
```

 With dumped .vcd file, I checked that the structural decoder corresponds with waveform.



Then, I built 4 input multiplexer with 2 NOT gates and 8 AND gates (4 for addresses and 4 for inputs & addresses), 2 OR gates (1 for in0 and in1, 1 for in2 and in3). Following is truth tables for behavioral and structural multiplexer. Then, I checked gtkwave.

<Behavioral>


```
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog multiplexer.v
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog multiplexer.t.v
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
```

A0	A1	A	B	C	D	Out	Expected Output
0	0	0	x	x	x	0	0
0	0	1	x	x	x	1	1
1	0	x	0	x	x	0	0
1	0	x	1	x	x	1	1
0	1	x	x	0	x	0	0
0	1	x	x	1	x	1	1
1	1	x	x	x	0	0	0
1	1	x	x	x	1	1	1

<Structural>

```
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog multiplexer.v
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog multiplexer.t.v
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
VCD info: dumpfile multiplexer.vcd opened for output.
```

A0	A1	A	B	C	D	Out	Expected Output
0	0	0	x	x	x	0	0
0	0	1	x	x	x	1	1
1	0	x	0	x	x	0	0
1	0	x	1	x	x	1	1
0	1	x	x	0	x	0	0
0	1	x	x	1	x	1	1
1	1	x	x	x	0	0	0
1	1	x	x	x	1	1	1

 

Red sections indicate null part of the logic (X)

Finally, I built FULL adder with 2 XOR gates, 2 AND gates and 1 OR gate. Followings are truth tables for behavioral and structural adder. Then, gtkwave result is checked with the truth tables.

<Behavioral>

```
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
```

A	B	Cin	S	Cout	ExpectedS	ExpectedC
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

<Structural>

```
mindew@mindew:~/Desktop/CompArch/HW2$ tverilog adder.v
mindew@mindew:~/Desktop/CompArch/HW2$ iverilog adder.t.v
mindew@mindew:~/Desktop/CompArch/HW2$ ./a.out
```

A	B	Cin	S	Cout	ExpectedS	ExpectedC
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

